

Damping Factor

Joey White

Hephaestus Audio

The effective output impedance of an amplifier is given by:

$$R_x = \frac{V_{O2} - V_{O1}}{\frac{V_{O1}}{R_{O1}} - \frac{V_{O2}}{R_{O2}}}$$

V_{O1} is the output level with load R_{O1}

V_{O2} is the output level with load R_{O2}

Note that in general this value is *frequency dependent*.

If $R_{O1} \rightarrow \infty$ (i.e. no load), then it can be simplified to:

$$R_x = \left(\frac{V_{O1}}{V_{O2}} - 1 \right) R_{O2}$$

If the load R_{O2} is the nominal 8Ω , then the 8Ω *damping factor* is given by:

$$DF = \frac{1}{\frac{V_{O1}}{V_{O2}} - 1}$$